














ELECTRICITY

Key Vocabulary		Components (Parts) Vocabulary		
electricity	The flow of an electric current through a material, e.g. from a power source through wires to an appliance .	cell: Normally, we would call this a battery but scientifically, this is a cell. Two or more cells joined together form a battery .	bulb: Lights up in a complete circuit .	buzzer: Makes a noise in a complete circuit .
appliances	A piece of equipment or a device designed to perform a particular job, such as a washing machine or mobile phone.			
battery	A device that stores electrical energy as a chemical. Two or more cells joined together form a battery .	wires: Used to connect the different components in the circuit together.	motor: Produces movement in a complete circuit .	switch: Used to turn other components in the circuit on or off.
circuit	A pathway that electricity can flow around. It is based around wires and a power supply. Examples of components (parts) you can add in to a circuit are bulbs, switches, buzzers and motors.			

<p>Series Circuit</p> <p>A circuit where the components are connected in a loop. Electricity flows through each component in a single pathway.</p> 	<p>Complete Circuit</p>  <p>Electricity can flow. The components will work.</p>	<p>Incomplete Circuit</p> <p>There is a break in the circuit that prevents the electricity from flowing. The components will not work.</p> 	<p>Switches can be used to open or close a circuit. When off, a switch 'breaks' the circuit to stop the flow of electricity. When on, a switch 'completes' the circuit and allows the electricity to flow.</p>  <p>push button switch</p>  <p>slide switch</p>
--	--	--	---


<p>Materials can be tested in a circuit to see if they are electrical conductors or electrical insulators.</p>  <p>10p = metal = electrical conductors</p> <p>test circuit</p> <p>ruler = plastic = electrical insulators</p>	<p>Key Vocabulary</p> <p>mains electricity Electricity supplied through wires to a building.</p> <p>electrical conductor A conductor of electricity is a material that will allow electricity to flow through it.</p> <p>electrical insulator Materials that are electrical insulators do not allow electricity to flow through them.</p>
--	--



Electricity can be extremely dangerous if it is not used safely. It can cause burns, shocks, serious injury and in extreme cases, death.

Some important Electrical safety tips

- Do not put fingers or other objects in a plug
- Never use anything with a cord or a plug around water
- Stay away from power stations and power lines
- Never place drinks near electrical items
- Do not overload a plug socket or extension cord
- Do not use an electrical item if the cord/ wire is broken
- Do not put batteries in your mouth or swallow them



What I will know by the end of the topic:

- How to identify common appliances that run on electricity.
- How to construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- How to identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- How to recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- How to recognise some common conductors and insulators, and associate metals with being good conductors.

What should I already know?

Electricity is a source of power/ energy that allows something to heat up, light up, move or produce sound. Electrical power can come from plugging something in or using a battery. Electricity can be dangerous. Electrical appliances have switches to turn them on and off.